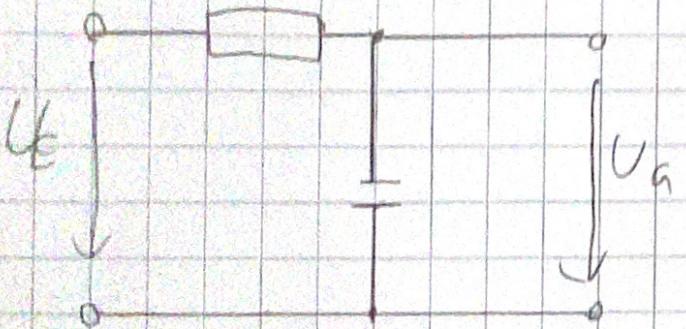


## Analoge Filter

### 2.1.1 Amplitudengang

Amplitudengang  $|G(j\omega)|$




Tief pass  
(filtert hohe Frequenzen heraus)

$$G(j\omega) = \frac{U_a}{U_e} = \frac{j\omega C}{R + j\omega C} = \frac{j\omega C}{R + \frac{1}{j\omega C}} = \frac{j\omega C}{j\omega C + 1} = \frac{1}{1 + j\omega RC}$$

$$|G(j\omega)| = \sqrt{1^2 + (\omega RC)^2}$$

$$A = 20 \log |G(j\omega)|$$

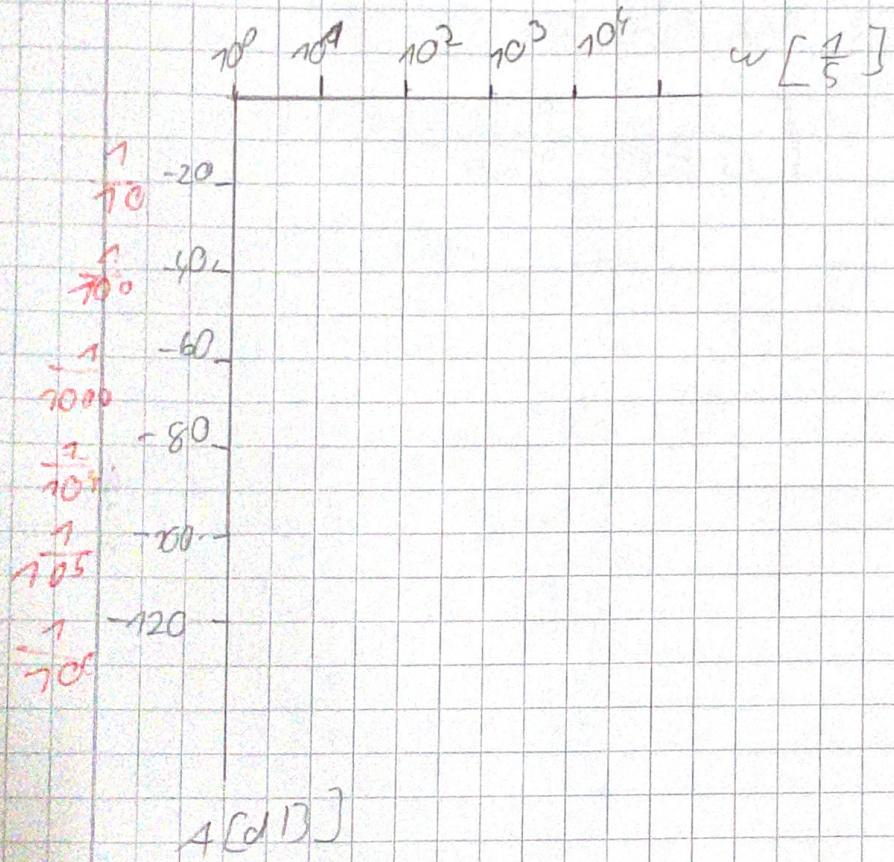

$A$  [dB]

Phasengang van  $G(j\omega)$

$$G(j\omega) = \frac{1}{1 + j\omega RC}$$

$$\varphi = \arctan \frac{0}{1} - \arctan \frac{\omega RC}{1}$$

$$\varphi = 0 - \arctan (\omega RC)$$

$$\varphi = -\arctan (\omega RC)$$

$$R = 10 \text{ k}\Omega$$

$$C = 10 \text{ nF}$$



Anpolstudiengang

$$\omega = 10, 20, 50, 100, 200, 500, 1000, \dots, 100\,000$$

$$A = 20 \log \left( \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \right)$$


$$\varphi = -\arctan(\omega R C)$$

$\omega$	$A$	$\varphi$
10	$-4,3 \cdot 10^{-6}$	
20	$-17,37 \cdot 10^{-6}$	
50	$-10,8 \cdot 10^{-6}$	
100	$-4,94 \cdot 10^{-6}$	-0,57
200	$-1,73 \cdot 10^{-5}$	-1,15
500	$-70,84 \cdot 10^{-5}$	-2,86
1000	$-47,21 \cdot 10^{-4}$	-5,7
2000	$-170,3 \cdot 10^{-4}$	-11,3
5000	$-969,1 \cdot 10^{-4}$	-26,57
10000	-3,01	-4,5
20000	-6,99	-63,45
50000	-14,75	-78,69
100000	-20,04	-84,29
200k		-87,14
500k		-88,86
1M		-89,93

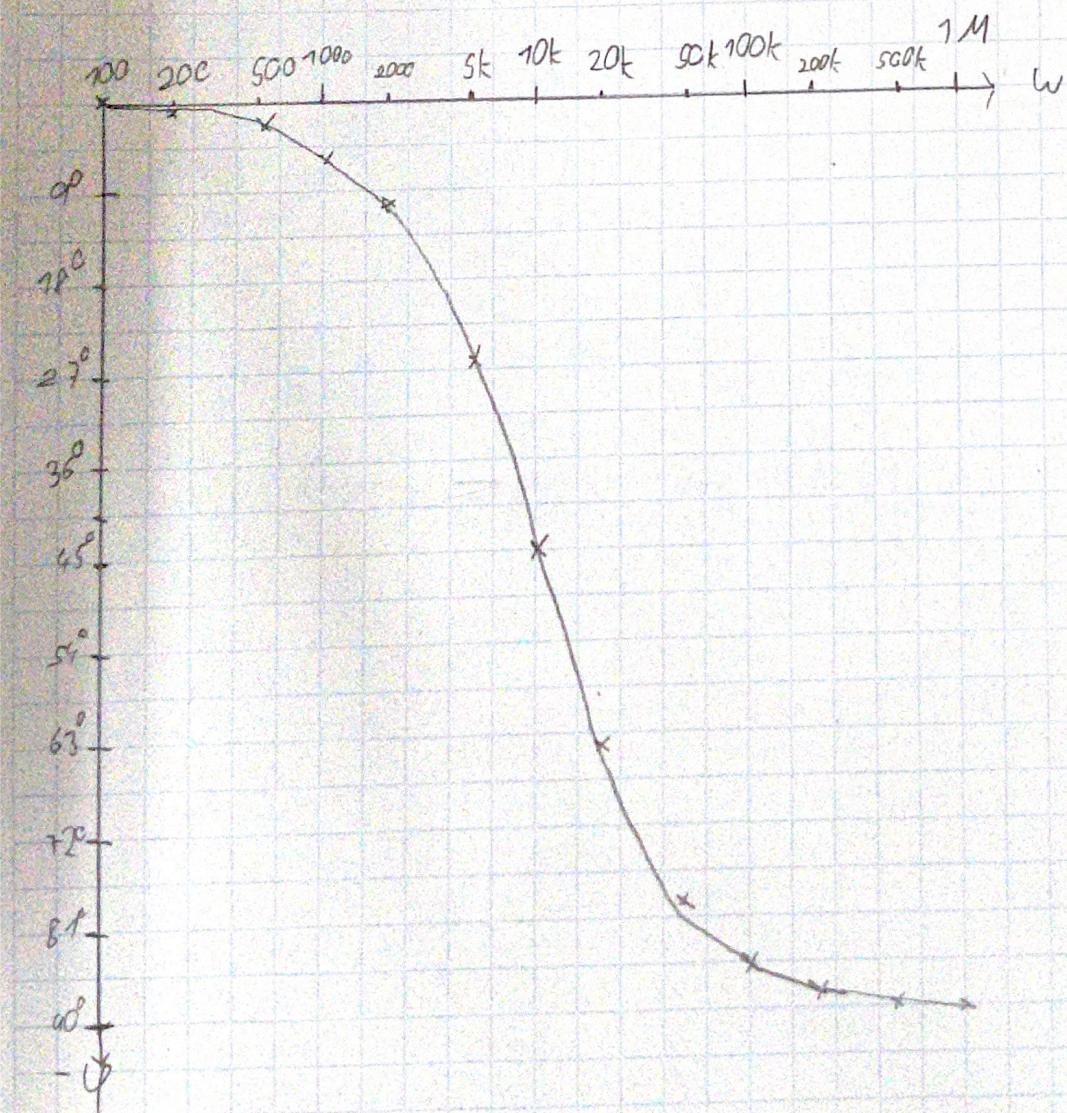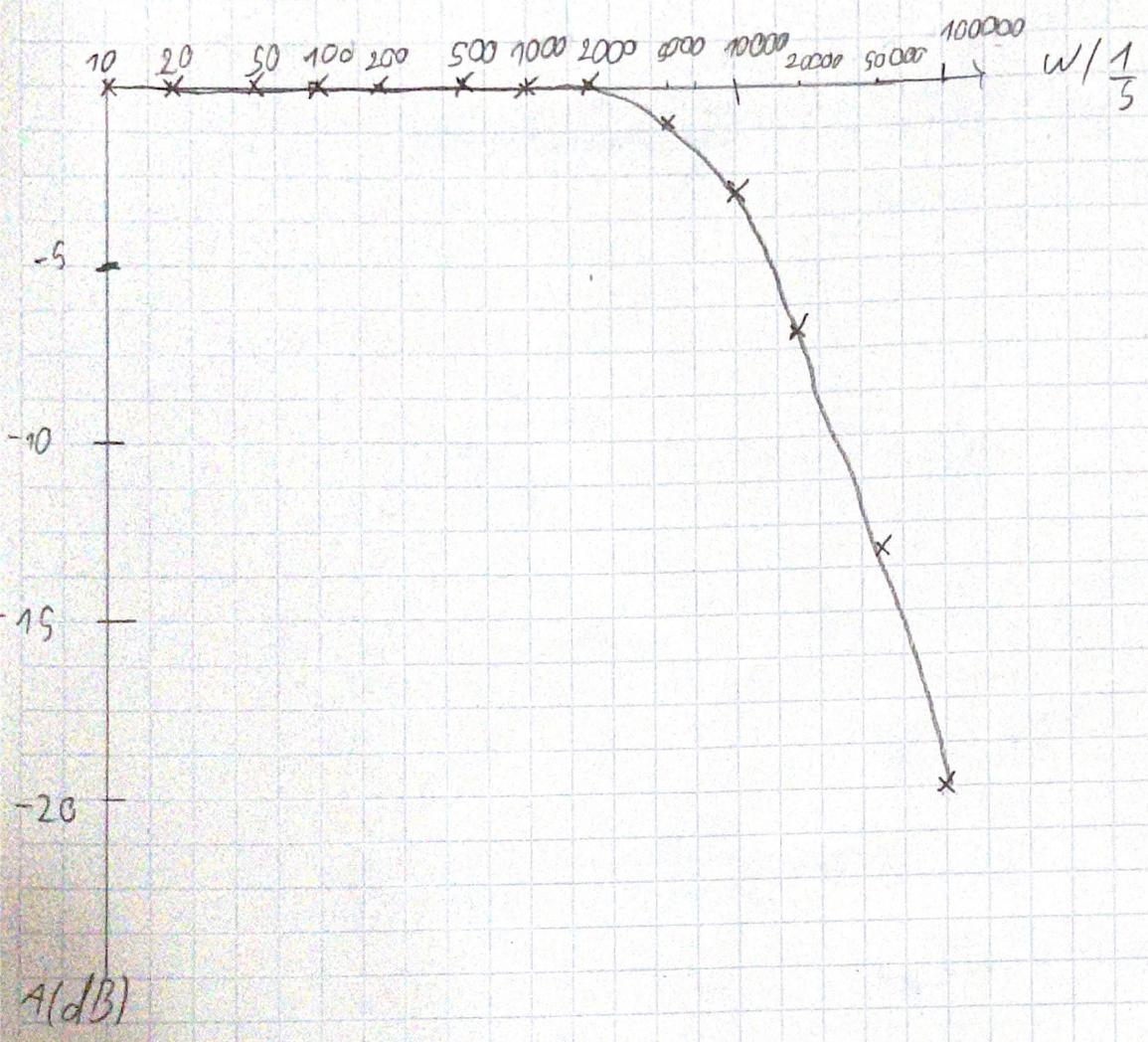
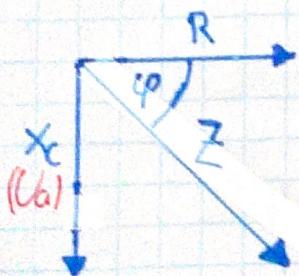
## Grenzfrequenz

-3dB Abschweichung  $U_a = \frac{1}{\sqrt{2}} \cdot U_E = 0,707 \cdot U_E$   
 $\sim 70\%$  von  $U_E$



$$\frac{U_a}{U_e} = \frac{1}{\sqrt{2}}$$

$$|m| = Re$$

$$\Rightarrow |\psi| = 45^\circ$$

$$G(j\omega) = \frac{1}{1 + j\omega RC} \Rightarrow |m| = Re$$

$$\omega_0 RC = 1 \Rightarrow \omega_0 = \frac{1}{RC}$$

Bsp.:  $f_0 = 10 \text{ Hz}$


$$\left( \omega_0 = \frac{1}{RC} \xrightarrow{\omega_0 \rightarrow 10^{-6}} 10^{-6} \right)$$

$$\omega_0 = 2\pi f_0 = 62,8 \frac{7}{5}$$

$$\text{Ann. } C = 1 \mu F$$

$$R = \frac{1}{\omega C} = \frac{1}{62,8 \frac{7}{5} \cdot 1 \cdot 10^{-6}} \approx 15,9 \text{ k}\Omega$$

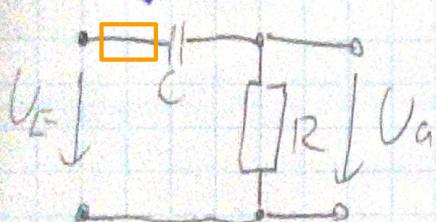Hochpass (filtert hohe Frequenzen heraus) KSN



$$X_C = \frac{1}{j\omega C}$$

$$R \cdot x = 1$$

$$x =$$

$$G(j\omega) = \frac{U_a}{U_E} = \frac{1}{j\omega C + R} = \frac{1}{j\omega R_C + 1} = \frac{1}{1 + \frac{j\omega}{R_C}}$$

$$|G(j\omega)| =$$

$$\varphi =$$


HÜ

Aufgabe:

Hochpass:  $f_g = \text{Geburtsdatum} \cdot 5 \text{ kHz}$

Amplitudengang

Phasengang

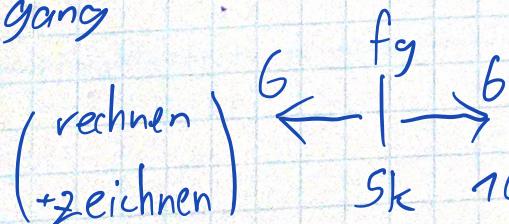

1) R, C

2) Tabelle (P)

$G(j\omega)$

dB

$\varphi$

w

4te Aufgabe

## Arbeitsauftrag:

$$f_g = 1 \cdot 5 \text{ kHz} = 5 \text{ kHz}$$

1)

$$R = \frac{1}{\omega C} = \frac{1}{31415,93 \cdot 1 \mu} = 31,83 \Omega$$

$$C = 1 \mu F$$

$$\omega = 2\pi f_g = 2\pi 5 \text{ kHz} = 31,415,93 \frac{1}{\text{s}}$$

2)

$\omega$	$ G(j\omega) $	$\varphi$
	dB	
$3141592,65$	$-0,43 \cdot 10^{-3}$	$-0,57$

$1256637,06$	$-2,71 \cdot 10^{-3}$	$-1,43$
--------------	-----------------------	---------

$628318,93$	$-10,8 \cdot 10^{-3}$	$-2,86$
-------------	-----------------------	---------

$314159,25$	$-43 \cdot 10^{-3}$	$-5,7$
-------------	---------------------	--------

$125663,71$	$-263,3 \cdot 10^{-3}$	$-14,03$
-------------	------------------------	----------

$62831,85$	$-969,1 \cdot 10^{-3}$	$-26,56$
------------	------------------------	----------

$31415,92$	$-3,01$	$-45$
------------	---------	-------

$12566,37$	$-8,60$	$-68,19$
------------	---------	----------

$6283,19$	$-14,15$	$-78,69$
-----------	----------	----------

$3141,59$	$-20,04$	$-84,29$
-----------	----------	----------

$1256,63$	$-27,97$	$-87,77$
-----------	----------	----------


$628,31$	$-33,48$	$-88,85$
----------	----------	----------

$314,16$	$-40$	$-89,42$
----------	-------	----------

$$|G(j\omega)| = 20 \log \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

$$\varphi = -\arctan \frac{1}{\omega RC}$$

T A B E L L E

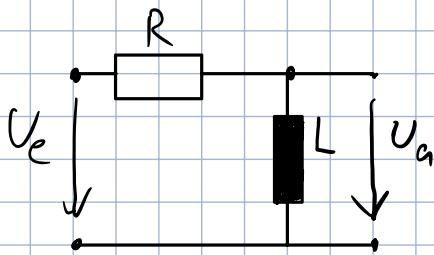

1)

$$G(j\omega) = \frac{U_a}{U_e} = \frac{j\omega L}{R + j\omega L} \cdot \frac{\frac{1}{j\omega L}}{\frac{1}{j\omega L}} = \frac{1}{1 + \frac{R}{j\omega L}} \rightarrow 1 - j \cdot \frac{R}{\omega L}$$


$$= \frac{|Z_N| \cdot e^{j\varphi_Z}}{|Z_N| j e^{j\varphi_N}} = \frac{e^{j\varphi_Z}}{e^{j\varphi_N}} = e^{j(\varphi_Z - \varphi_N)}$$

$$|G(j\omega)| = \sqrt{\gamma^2 - \alpha^2} = \sqrt{1 + (\frac{R}{\omega L})^2}$$

$$\varphi = 0 - \arctan\left(-\frac{R}{1}\right) = 0 - \arctan\left(-\frac{R}{\omega L}\right)$$

$$k = 1$$

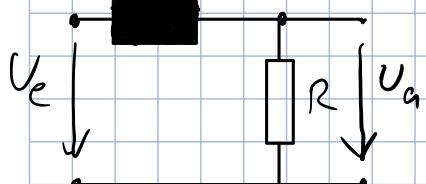
$$w_G \dots Re = 1 \text{ m} \Rightarrow \frac{R}{\omega L} = \frac{1}{1} \Rightarrow w_G = \frac{R}{L}$$



$$G(j\omega) = \frac{U_a}{U_e} = \frac{R}{R + j\omega L} \cdot \frac{\frac{1}{R}}{\frac{1}{R}} = \frac{1}{1 + j \frac{\omega L}{R}}$$

$$|G(j\omega)| = \sqrt{1^2 + (\frac{\omega L}{R})^2}$$
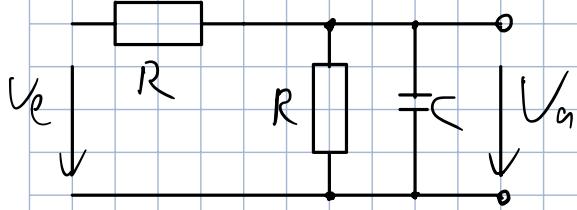
$$\varphi = 0 - \arctan\left(\frac{\omega L}{R}\right)$$



$$G(j\omega) = \frac{1}{1 + \dots}$$


$$G(j\omega) = \frac{U_a}{U_e} = \frac{R \parallel X_C}{R + R \parallel X_C} = \frac{\frac{1}{R} + j\omega C}{R + \frac{1}{R} + j\omega C} \cdot \frac{\frac{1}{R} + j\omega C}{\frac{1}{R} + j\omega C}$$

$$= \frac{1}{\frac{R}{R} + j\omega RC + 1} = \frac{1}{2 + j\omega RC} = \frac{1}{2 + j\omega \frac{RC}{2}}$$

$\varphi = \arctan \left( \frac{0}{1} \right) - \arctan \left( \frac{j\omega \frac{RC}{2}}{2} \right) \Rightarrow \varphi = -\arctan \left( \frac{\omega RC}{2} \right)$

$$|G(j\omega)| = \frac{1}{\sqrt{1^2 + (\frac{\omega RC}{2})^2}}$$
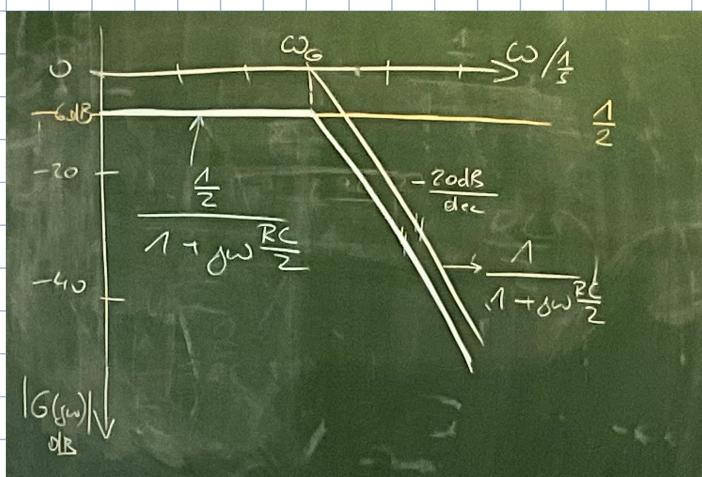
$$1 = \omega_g \frac{RC}{2} \Rightarrow \omega_g = \frac{1}{\frac{RC}{2}} = \frac{2}{RC}$$



Bsp.




$$G(j\omega) = \frac{V_a}{V_e} = \frac{\frac{R_2}{R_1 + j\omega R_2 C}}{\frac{R_2}{R_1 + j\omega R_2 C}} \cdot \frac{\frac{1 + j\omega R_2 C}{1 + j\omega R_2 C}}{\frac{1 + j\omega R_2 C}{1 + j\omega R_2 C}} =$$

$$= \frac{R_2}{R_1 + j\omega R_2 C R_1 C + R_2} = \frac{R_2}{R_1 + R_2 + j\omega R_1 R_2 C} \cdot \frac{\frac{1}{R_1 + R_2}}{\frac{1}{R_1 + R_2}} = \frac{\frac{R_2}{R_1 + R_2}}{1 + j\omega \frac{R_1 R_2 C}{R_1 + R_2}}$$

$$\Rightarrow G(j\omega) = \frac{\frac{R_2}{R_1 + R_2}}{1 + j\omega \frac{R_1 R_2 C}{R_1 + R_2}}$$

Bsp: 24. 11. 2021

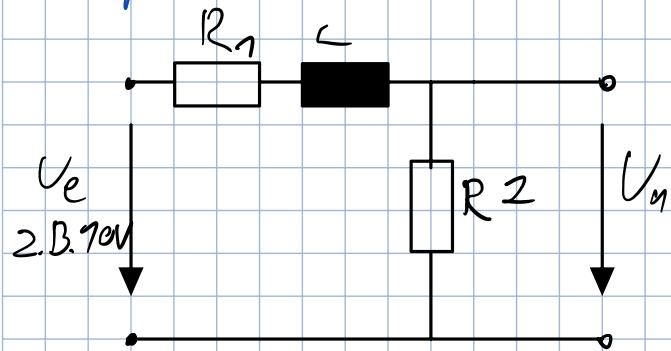

$\omega \ll \omega_L$

$\omega > \omega_L$

$x_L \ll \omega L$

$x_L > \omega L$

$$\frac{V_{a, \text{max}}}{V_e} = \frac{R_2}{R_1 + R_2}$$

$$V_{a, \text{max}} = V_C \frac{R_2}{R_1 + R_2} \quad (\omega = 0)$$

$$G(j\omega) = \frac{V_a}{V_e} = \frac{\frac{R_2}{R_1 + R_2 + X_L}}{\frac{1}{R_1 + R_2}} =$$

$$= \frac{R_2}{R_1 + R_2 + j\omega L} \cdot \frac{1}{\frac{1}{R_1 + R_2}} =$$

$$= \frac{\frac{R_2}{R_1 + R_2}}{1 + j\frac{\omega L}{R_1 + R_2}}$$

$$= \frac{\frac{R_2}{R_1 + R_2}}{1 + j\frac{\omega L}{R_1 + R_2}}$$

$$|G(j\omega)| = \sqrt{(R_1 + R_2)^2 + (\omega L)^2}$$


$$\textcircled{1} \quad \omega_g : R_1 + R_2 - \omega g L \Rightarrow \omega_g = \frac{R_1 + R_2}{L}$$

$$\textcircled{2} \quad \varphi = -\arctan \left( \frac{\omega L}{R_1 + R_2} \right)$$

$$\textcircled{2} \quad 1 = \frac{\omega g L}{R_1 + R_2} \Rightarrow \omega g = \frac{R_1 + R_2}{L}$$

$$\textcircled{2} \quad \varphi = -\arctan \frac{\omega L}{R_1 + R_2} = -\arctan \frac{\omega L}{R_2 + R_2}$$

Bsp.:

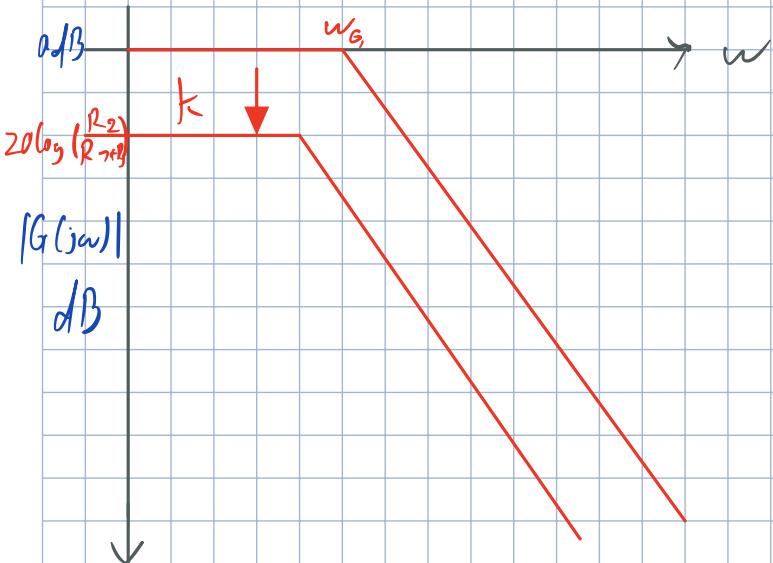

f<sub>g</sub>: Geburtsstag: 7.04 Monat

10<sup>0</sup>

02

74 Hz ... 30 kHz

10.2

$$f_g = 1000^2 \text{ Hz}$$

$$R_1, R_2, h$$

$$\text{ann.: } L = 27 \text{ mH}$$

$R_1, R_2$  errechnen

Bodediagramm / Phasengang



SIMULATION LTSPICE

$$f_g = 1 \cdot 10 + 0.5 = 1005 \text{ Hz}$$

$$\omega_g = 2\pi f_g = 6314,6 \frac{1}{3}$$

$$R_1 = 100 \Omega$$
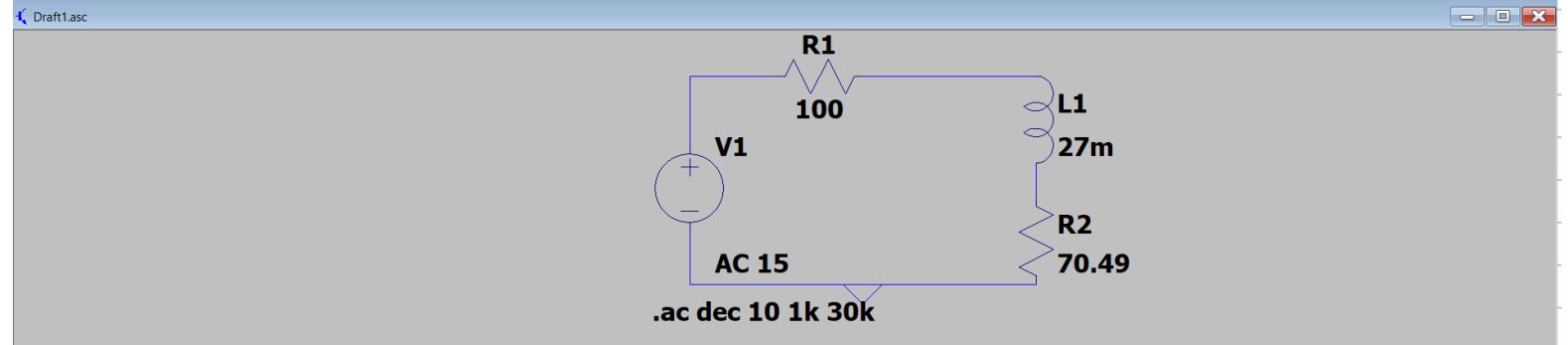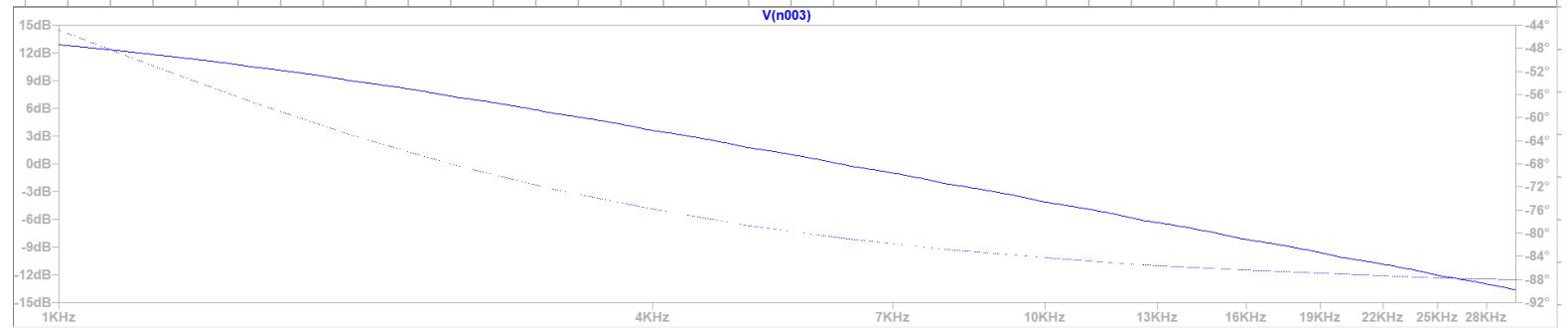
$$\omega_g \cdot L = R_1 + R_2 \rightarrow R_2 = \omega_g \cdot L - R_1 = 6314,6 \frac{1}{3} \cdot 27 \text{ mH} - 100 \Omega = 70,49 \Omega$$



## Zusammengesetzte Frequenzgänge



$$G(j\omega) = U_a - G_1(j\omega)$$

$$U_a = U_{a1} \cdot G_2(j\omega)$$

$$U_a = U_c \cdot G_1(j\omega) - G_2(j\omega) \Leftrightarrow \frac{U_a}{U_c} = G_1(j\omega) \cdot G_2(j\omega)$$

Bsp:  $G_1(j\omega) = 100$

$G_2(j\omega) = 1000$

$$G(j\omega) = 100 \cdot 1000 = 100000$$


$$10^2 \quad 10^3 \quad 10^{2+3} = 10^5$$

$$\log|G(j\omega)| = \log|G_1(j\omega)| + \log|G_2(j\omega)|$$

Bsp:



Bsp.: HP, TP

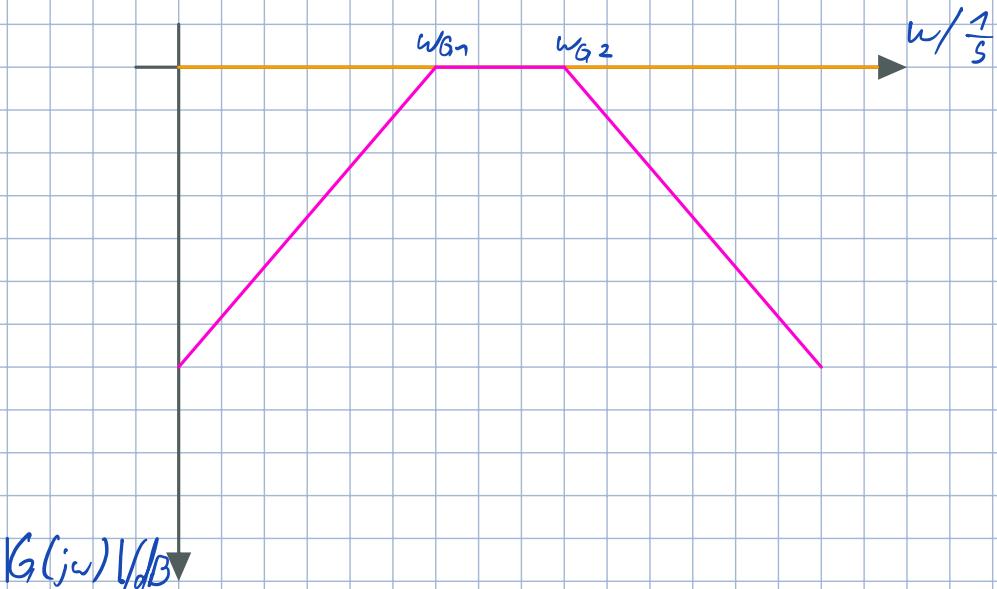

Bsp.: phasenanhäufendes System

$$G(j\omega) = \frac{1 + j\omega T_1}{1 + j\omega T_2} = \underbrace{(1 + j\omega T_1)}_{G_1(j\omega)} \cdot \underbrace{\frac{1}{1 + j\omega T_2}}_{G_2(j\omega)}$$

$$T_1 = 1, \quad T_2 = 0,2$$


$$|G(j\omega)| = \sqrt{\frac{(1+\omega T_1)^2}{(1+\omega T_2)^2}}$$

$$\varphi = \arg(G(j\omega)) = \arctan(\omega T_1) - \arctan(\omega T_2)$$


Grenzfrequenzen (Knickfrequenz)

$$\omega_{G_1} = \frac{1}{T_1} = 1 \quad \omega_{G_2} = \frac{1}{0,2} = 5$$

Ampelbildung amy

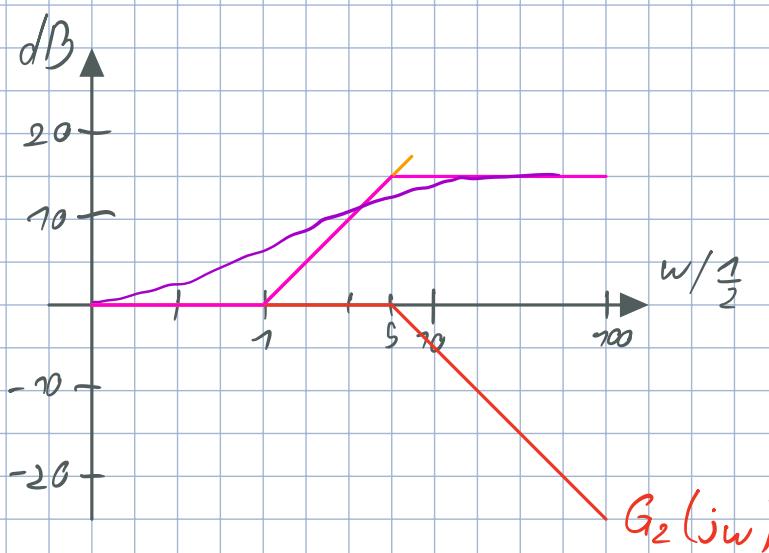

# Phasengang

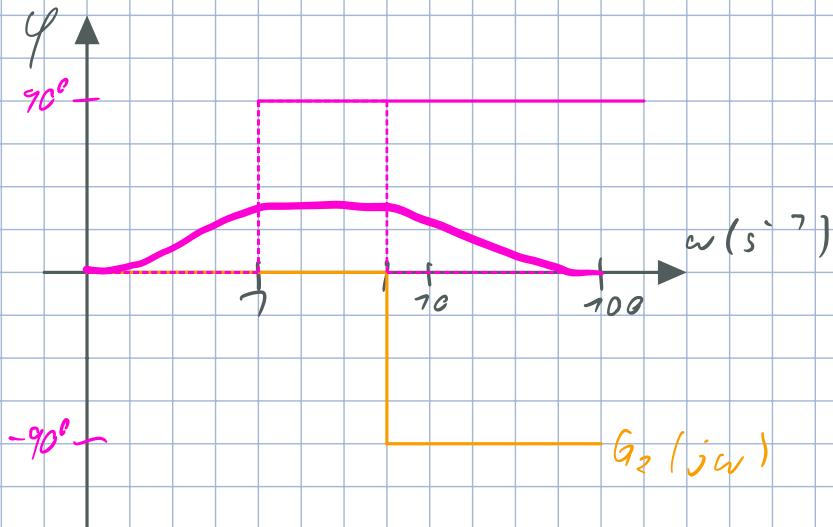


Maximum trifft im geometrischen Mittel  $\omega$  auf

$$\omega_m = \frac{1}{\sqrt{T_1 T_2}} = \sqrt{5}$$

$$\varphi_{\max}|_{\omega=\omega_m} = \arctan \sqrt{\frac{T_1}{T_2}} - \arctan \sqrt{\frac{T_2}{T_1}} = 47,8^\circ$$

Bsp.:

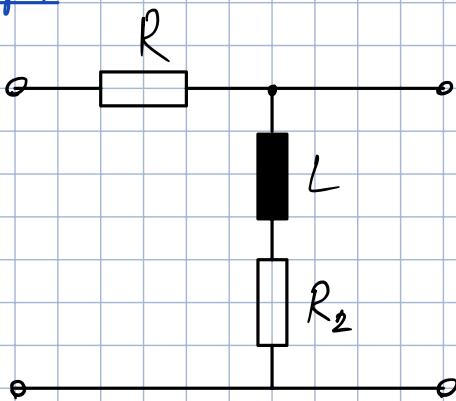

ges:  $G(j\omega)$ ,  $\omega_0$ ,  $\omega_{Q2}$ ,  $k$ ,  $\varphi$


$$k \cdot \frac{1 + j\omega}{1 + j\omega_0} \quad k \dots \text{nicht } \omega \text{-abhängig}$$

$$k = \frac{R_2}{R_1 + R_2}$$

$$G(j\omega) = \frac{U_a}{U_e} = \frac{R_2 + j\omega L}{R_1 + R_2 + j\omega L} = \frac{R_2 \cdot (1 + j\frac{\omega L}{R_2})}{R_1 + R_2 \left(1 + j\frac{\omega L}{R_1 + R_2}\right)} = \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\frac{\omega L}{R_2}}{1 + j\frac{\omega L}{R_1 + R_2}}$$

$$\varphi = \arctan \left( \frac{\omega L}{R_2} \right)$$

Bsp.

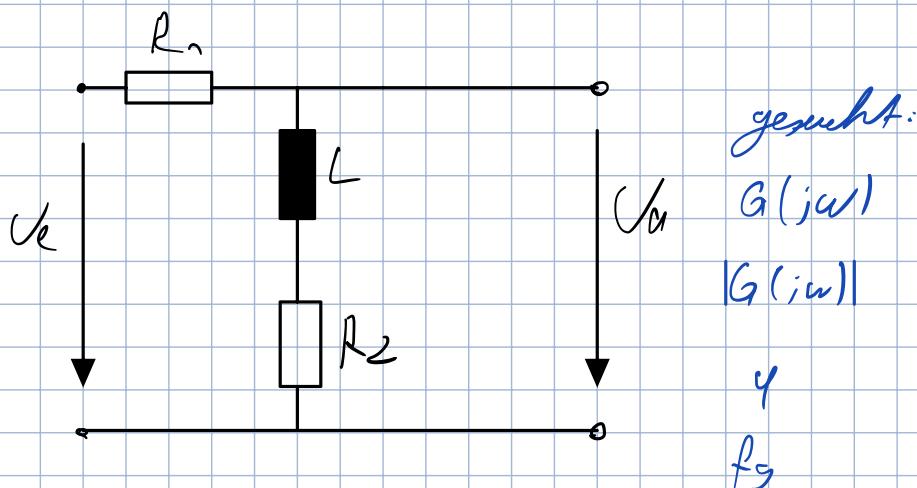

- Bodediagramm
- Phasengang

$$k = \frac{R_2}{R_1 + R_2}$$

$$G(j\omega) = \frac{U_a}{U_e} = \frac{R_2 + j\omega L}{R_1 + R_2 + j\omega L} = \frac{R_2}{R_1 + R_2} \cdot \underbrace{\frac{1 + j \frac{\omega L}{R_2}}{1 + j \frac{\omega L}{R_1 + R_2}}}_{k}$$

$$|G(j\omega)| = \sqrt{R_2^2 + \omega^2 L^2}$$

$$\varphi = \arctan\left(\frac{\omega L}{R_2}\right) - \arctan\left(\frac{\omega L}{R_1 + R_2}\right)$$

Annahme:

$$L = 100 \text{ mH} \quad \omega_{B1} = 10 \text{ k} \frac{1}{s} \quad \omega_{B2} = 100 \text{ k} \frac{1}{s}$$

$$\omega = 70, 100, 1k, 10k, 100k, 1M, 10M$$


$$I_m = R_1 \Rightarrow R_2 = \omega L = 10 \text{ k} \frac{1}{s} \cdot 100 \text{ mH} = 1 \text{ k} \Omega$$

$$I_m = R_m \Rightarrow R_1 + R_2 = \omega L = R_1 = \omega L - R_2 = 100 \text{ k} \frac{1}{s} \cdot 100 \text{ mH} - 1 \text{ k} \Omega = 9 \text{ k} \Omega$$

$$f_g = \frac{\omega_{B1}}{2\pi} = \frac{10 \text{ k} \frac{1}{s}}{2\pi} = 791,5 \text{ Hz} \approx 7,9 \text{ kHz}$$

$$f_g = \frac{\omega_{B2}}{2\pi} = \frac{100 \text{ k} \frac{1}{s}}{2\pi} = 7915,5 \text{ Hz} \approx 79,2 \text{ kHz}$$

$\omega$	$20 \log  G(j\omega) $	$\varphi$
10	-20 dB	0,057°
100	-19,9995 dB	0,516°
1k	-19,9572 dB	5,137°
10 k	-17,03 dB	39,3°
100 k	-2,967 dB	39,3°
1M	-0,043 dB	5,137°
10M	-0,00043 dB	0,517°

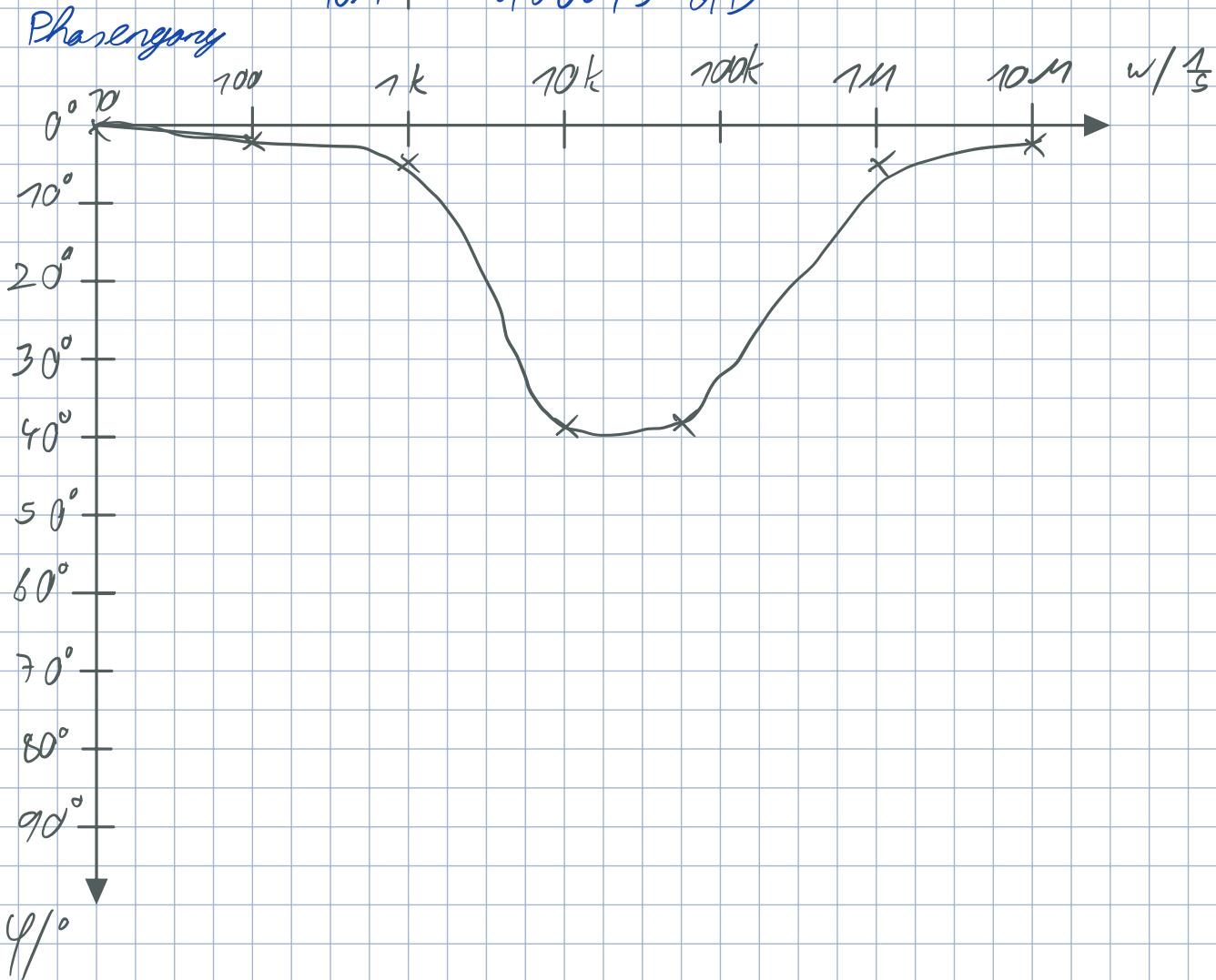

Amplified energy

